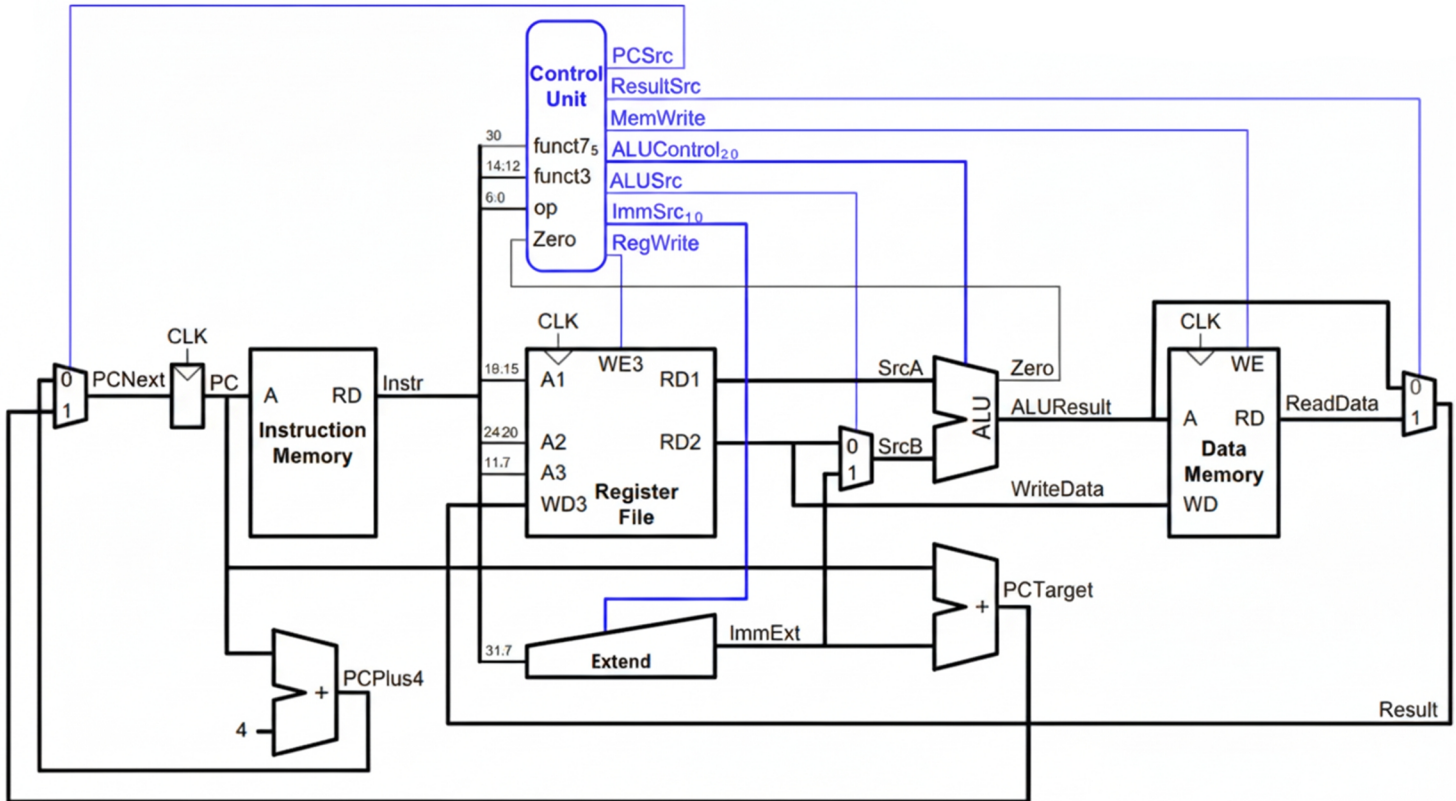


معماری کامپیوتر - تمرین کامپیوتری دوم

طراحی دیتاپس:



طراحی کنترلر:

Instruction	▼	Opcode	▼	RegWrite	▼	ImmSrc	▼	ALUSrc	▼	MemWrite	▼	ResultSrc	▼	Branch	▼	ALUOp	▼
R-type (add, sub, ...)		110011		1		XX		0		0		0		0		10	
I-type (lw)		11		1		0		1		0		1		0		0	
S-type (sw)		100011		0		1		1		1		XX		0		0	
B-type (beq)		1100011		0		10		0		0		XX		1		1	
I-type (addi)		10011		1		0		1		0		0		0		10	
J-type (jal)		1101111		1		11		X		0		10		0		XX	